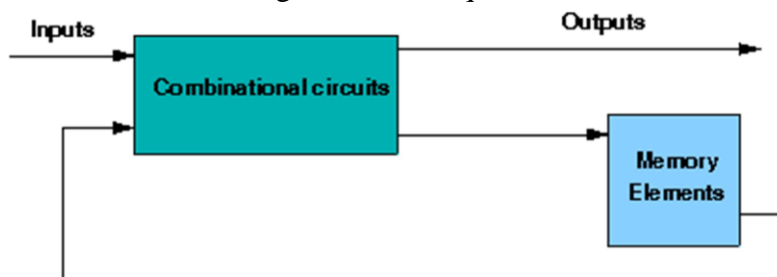


PRACTICAL-6

AIM : Registers and Counters

Theory

Design of Registers and Counters :- In a sequential circuit the present output is determined by both the present input and the past output. In order to receive the past output some kind of memory element can be used. The memory element commonly used in the sequential circuits are time-delay devices. The block diagram of the sequential circuit –




A circuit with flip-flops is considered a sequential circuit even in the absence of combinational logic. Circuits that include flip-flops are usually classified by the function they perform. Two such circuits are registers and counters:

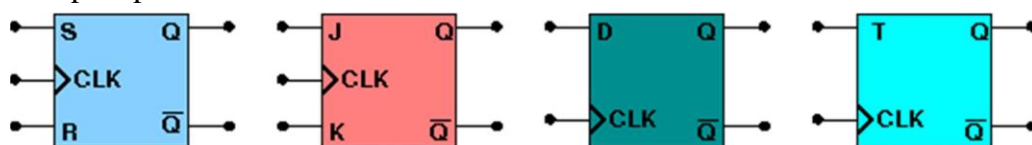1. Register is a group of flip-flops. Its basic function is to hold information within a digital system so as to make it available to the logic units during the computing process.
2. Counter is essentially a register that goes through a predetermined sequence of states.

There are various different kind of Flip-Flops. Some of the common flip-flops are:

R-S Flip-Flop, D Flip-Flop, J-K Flip-Flop, T Flip-Flop. The block diagram of different flip-flops are shown here –



RS flipflop If R is high then reset state occurs and when S=1 set state. the both cannot be high simultaneously. this input combination is avoided.

JK flipflop If J and K are both low then no change occurs. If J and K are both high at the clock edge then the output will toggle from one state to the other.

Truth Table				
J	K	CLK	Q	
0	0	↑	Q_0 (no change)	
1	0	↑	1	
0	1	↑	0	
1	1	↑	\bar{Q}_0 (toggles)	


D flipflop The D flip-flop tracks the input, making transitions with match those of the input D. It is used as data store.

Tflipflop The T or "toggle" flip-flop changes its output on each clock edge,

Types of Registers:


- **4-bit Serial-in Serial-out**

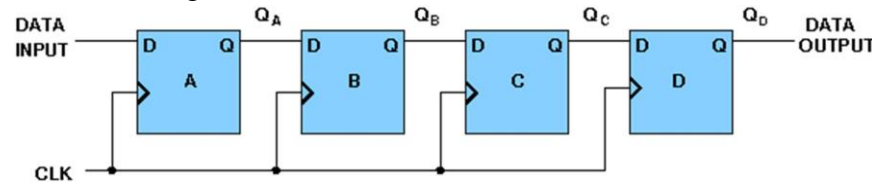4-bit serial-in serial-out register accepts digital data serially that is one bit at the time on one line. It produces the stored information on its output also in serial form. This is a shift register, as The binary number is "Shifted" one bit at time from one flip flop to the next. The block diagram is




- **4-bit Serial-in Parallel-out**

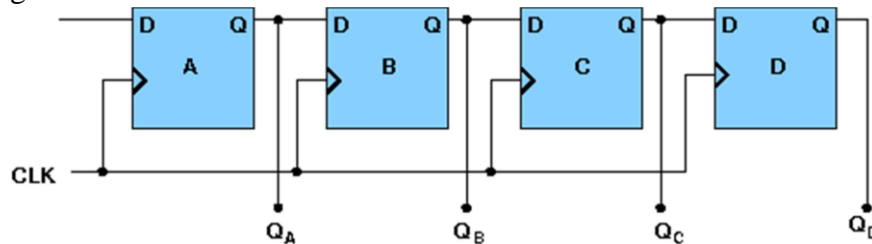In serial-in parallel-out register the data are loaded serially and read out in parallel. The block diagram is-




- **4-bit Parallel-in Serial-out**

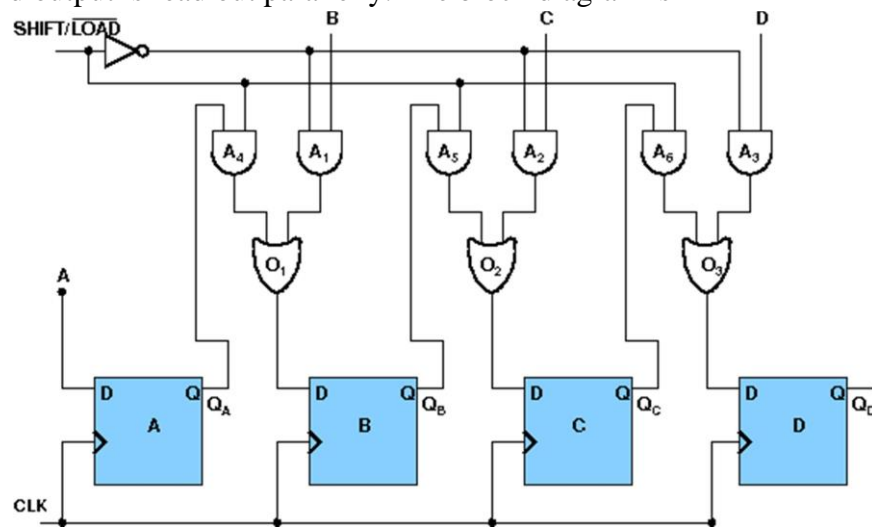In parallel-in serial out register the bits are entered simultaneously into their respective stages on parallel-lines, rather than on a bit-by- bit basis on one line as with serial data inputs and output is read out parallelly. The block diagram is-



- **4-bit Parallel-in Parallel-out**

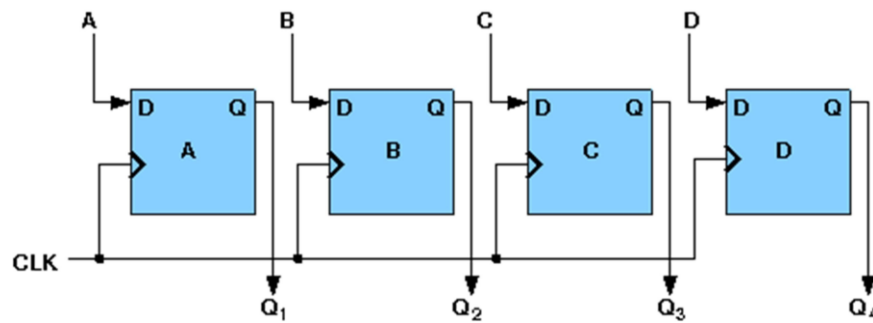
In parallel-in parallel out register the data is loaded in parallel and shifted out serially. The block diagram is-



Types of Counters:


- **4-bit Synchronous Binary Counter**


A counter is a sequential circuit that moves through a predefined sequence of states upon applying of clock pulses. The sequence of states may follow the binary number sequence or an arbitrary manner (no sequence). The simplest example of a counter is the binary counter which follows the binary number sequence. An n -bit binary counter contains n flip-flops and can count binary numbers from 0 to $(2^n - 1)$ (up counter which is incremental, if it counts decremental it is then down counter). logic diagram of 4 bit synchronous counter-

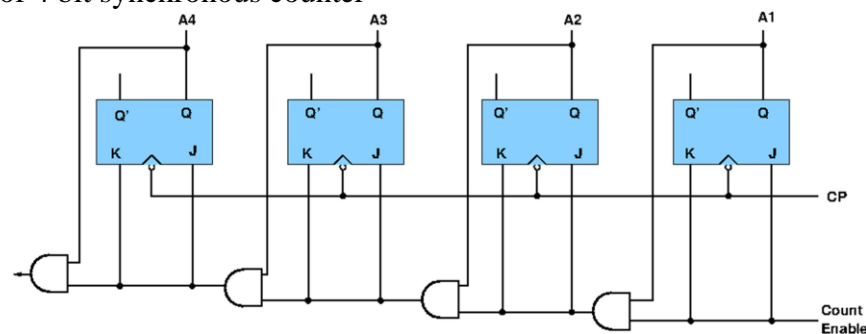

- **4-bit Synchronous Ring Counter**


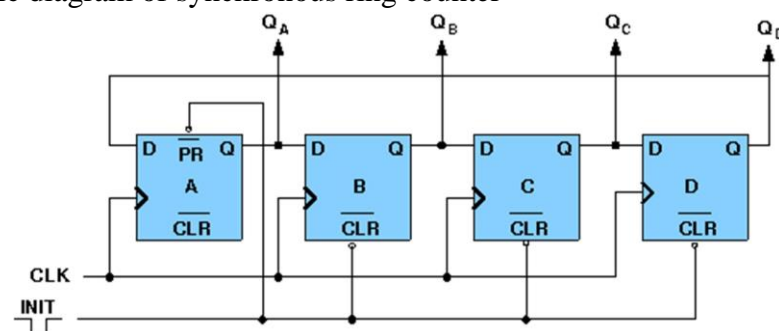
If the output of a shift register is fed back to the input, a ring counter results. The data pattern contained within the shift register will recirculate as long as clock pulses are applied. logic diagram of synchronous ring counter-



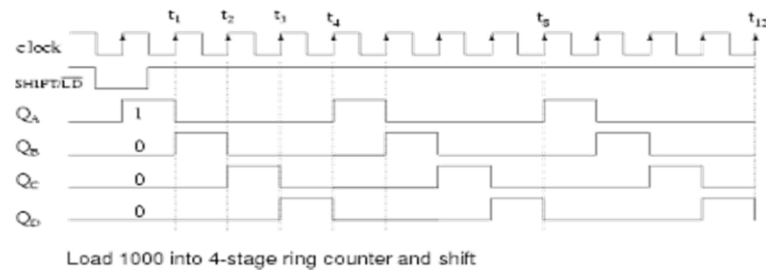Timing diagram:

- 4-bit Synchronous Johnson Counter**

If the complement output of a ring counter is fed back to the input instead of the true output, a Johnson counter results. This "reversed" feedback connection has a profound effect upon the behavior of the otherwise similar circuits. Recirculating a single 1 around a ring counter divides the input clock by a factor equal to the number of stages. Whereas, a Johnson counter divides by a factor equal to twice the number of stages. logic diagram of synchronous Johnson counter-

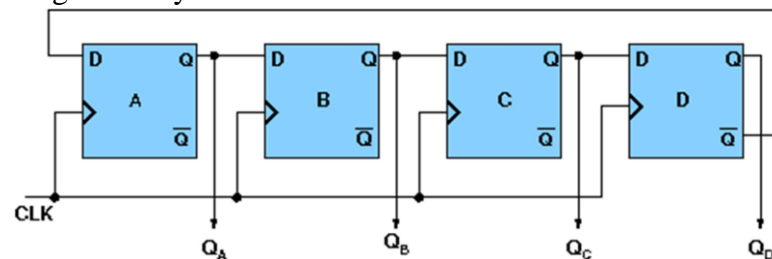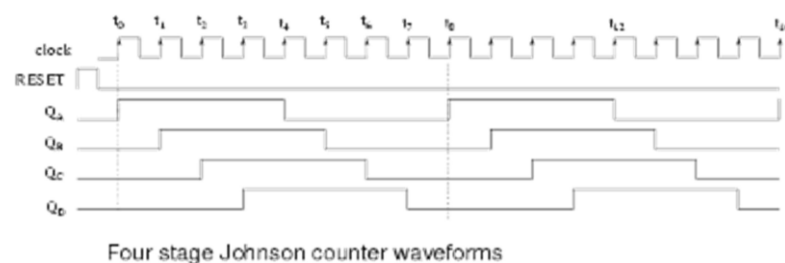**Timing Diagram-****Objective****Objective of designing registers:**

to understand the shifting of data

to examine the behavior of different modes of data input and data output(serial-in serial-out, serial-in parallel-out, parallel-in serial out,parallel-in parallel-out)

to make use of shift register in data transfer

developing skills in the designing and testing of sequential logic circuits

developing skills in analysing timing signals

Objective of designing counters:

Recommended learning activities for the experiment: Learning activities are

designed in two stages, a basic stage and an advanced stage. Accomplishment of

each stage can be self-evaluated through the given set of quiz questions consisting of

multiple type and subjective type questions. In the basic stage, it is recommended to perform the experiment firstly, on the given encapsulated working module, secondly, on the module designed by the student, having gone through the theory, objective and procedure.

It is recommended to perform the experiments following the given guideline to check behavior and test plans along with their own circuit analysis. Then students are recommended to move on to the advanced stage. The advanced stage includes the accomplishment of the given assignments which will provide deeper understanding of the topic with innovative circuit design experience. At any time, students can mature their knowledge base by further reading the references provided for the experiment.

color configuration of wire for 5 valued logic supported by the simulator:

if value is UNKNOWN, wire color= maroon

if value is TRUE, wire color= blue

if value is FALSE, wire color= black

if value is HI IMPEDENCE, wire color= green

if value is INVALID, wire color= orange

Test plan:

Give input and free running clock to the shift register as 10101 and check whether after 5 clock operation register output is set or not.

Take a mod-6 counter. use free running clock and check whether after 6 clock operation register output is set or not.

Procedure

Design of Registers and Counters:

Guideline to perform the experiment: Designing 4 bit shift register(serial in serial out)

1> Start the simulator as directed. This simulator supports 5-valued logic.

2> To design a 4 bit shift register (right shift), we need 4 MSD flipflop, 1 free running clock, 1 Bit switch (which will act as input to the left most flipflop), 4 Bit display(to see the output of individual flipflops so that the shifting can be seen with the clock input), wires.

3> The MSD flipflop component is in the sequential circuit drawer in the pallet. The pin configuration is shown whenever the mouse is hovered on any canned component of the palette or press the 'show pinconfig' button. Pin numbering starts from 1 and from the bottom left corner(indicating with the circle) and increases anticlockwise.

4> For MSD flipflop input is in pin-5, output(Q) is in pin-4, clock is in pin-8

5> click on the MSD flipflop component in the pallet and then click on the position of the editor window where you want to add the component(no drag and drop, simple click will serve the purpose), likewise add 4 MSD flipflops, 1 free running clock, 1 Bit switch and 4 bit Displays(from Display and Input drawer of the pallet, if it is not seen scroll down in the drawer)

6> To connect any two components select the Connection menu of Palette, and then click on the Source terminal and click on the target terminal. connect all the components, connect the clock to the pin-8 of all the MSD flipflops, connect a bit

switch to the pin-5(Q) of the left most MSD flipflop, connect 4 bit displays to the pin-4 of 4 MSD flipflops, connect the Q output of the previous flipflop to the D(pin5) input of the next flipflop.

7> To see the circuit working, click on the Selection tool in the pallet then give input by double clicking on the bit switch, to the left most D flipflop at pin-5(let it be 1), start the clock now check the output and see how the 1 is shifting from left to right.

Components :


To build any register or counters, we need :

1. Flip-Flops.
2. Logic Gates.
3. Wires to connect.



In case of counters the number of flip-flops depends on the number of different states in the counter.

Assignment Statements :

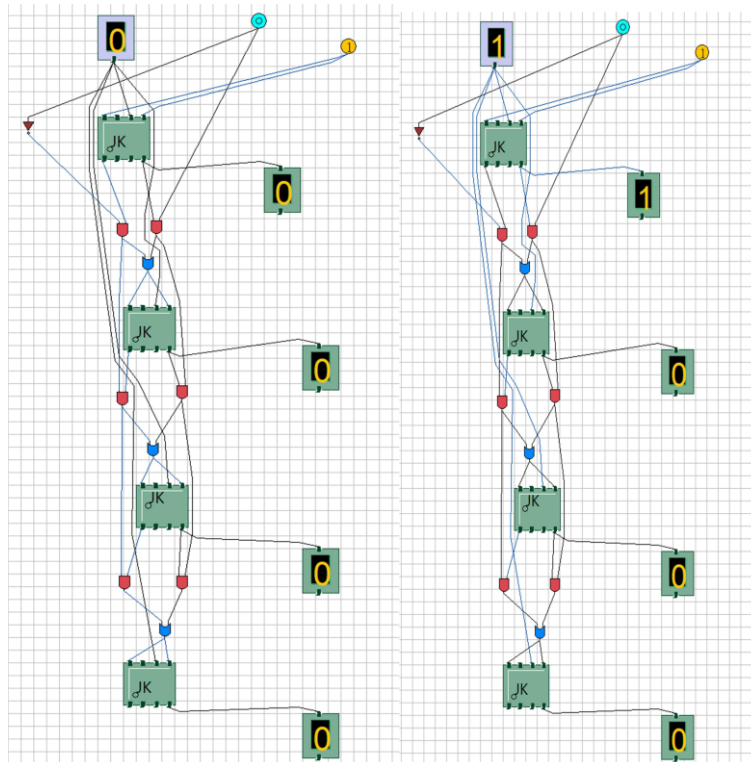
1. Design 4-bit synchronous up and down counter.



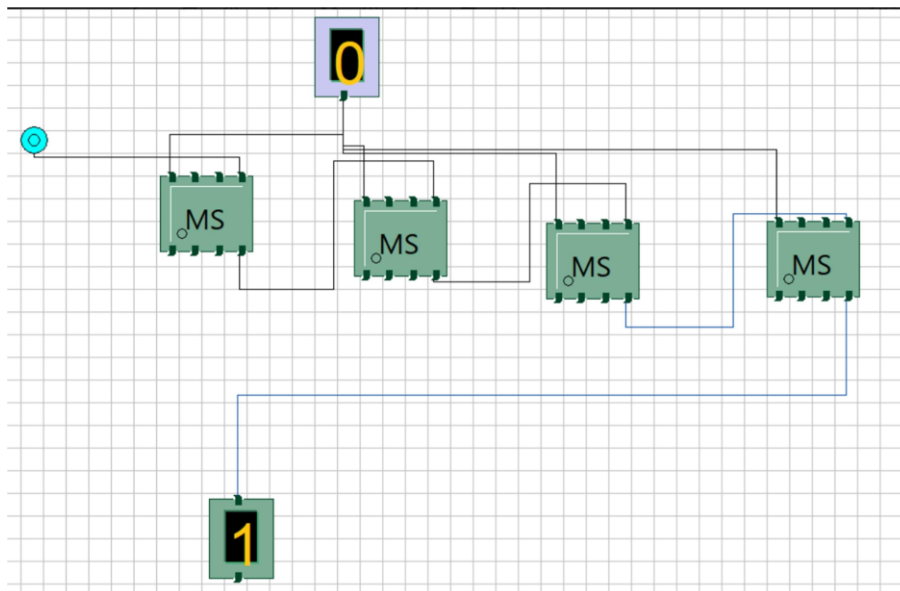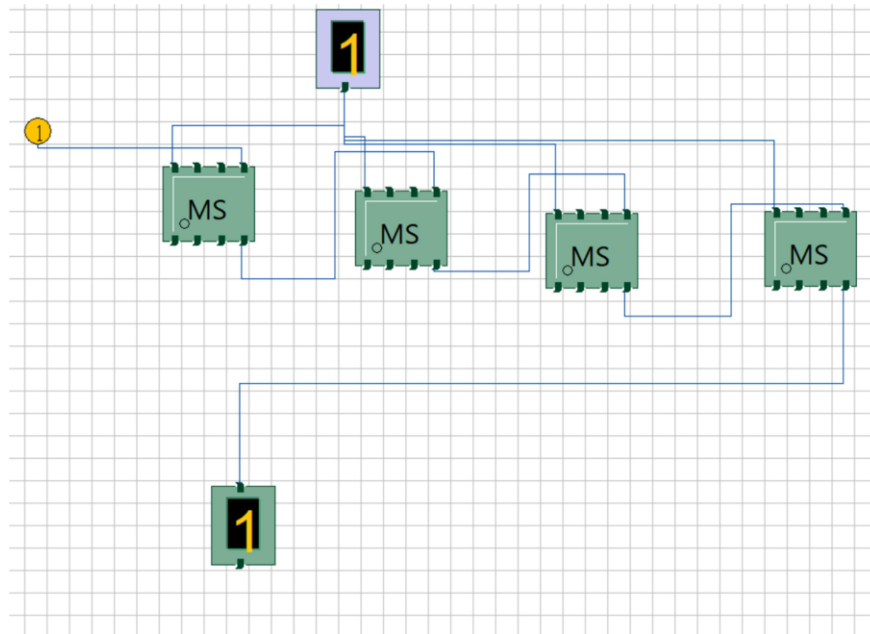2. Design a 5-bit Shift Registers using the flip-flops and check the output.



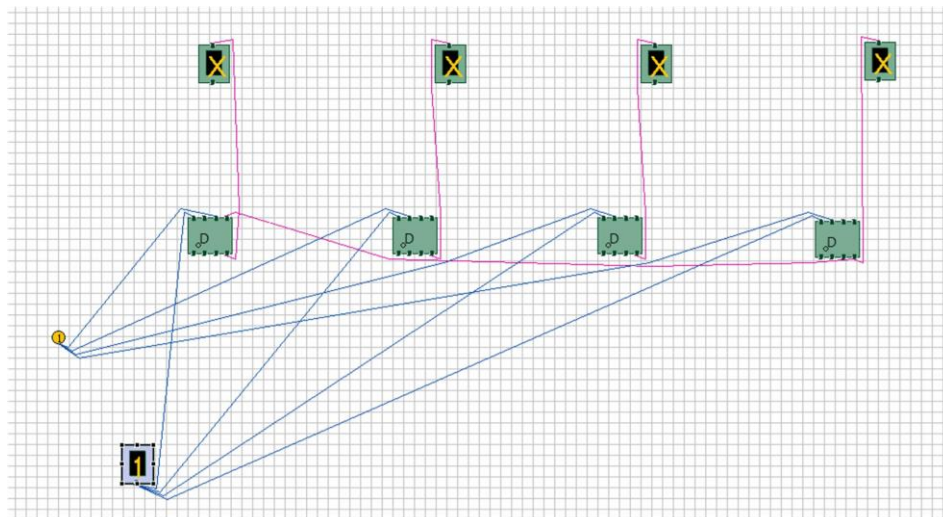3. Design a 5-bit ring counter and a johnson counter.



4. Design a mod-6 counter.

